

UEC750: Tutorial Sheet-6

1. For the CMOS inverter with a power supply voltage of $V_{DD} = 5 \text{ V}$, determine the fall time which is defined as the time elapsed between the time point at which $V_{out} = V_{90\%} = 4.5 \text{ V}$ and the time point at which $V_{out} = V_{10\%} = 0.5 \text{ V}$. Use both the average-current method and the differential equation method for calculating fall time. The output load capacitance is 1 pF . The nMOS transistor parameters are given as: $\mu_n C_{ox} = \frac{20 \mu\text{A}}{\text{V}^2}, \frac{W}{L} = 10, V_{t0,n} = 1 \text{ V}$.

2. Consider a CMOS inverter with the following parameters:

$$\begin{aligned} V_{T0,n} &= 1.0 \text{ V} \\ V_{T0,p} &= -1.2 \text{ V} \end{aligned}$$

$$\begin{aligned} \mu_n C_{ox} &= 45 \mu\text{A}/\text{V}^2 \\ \mu_p C_{ox} &= 25 \mu\text{A}/\text{V}^2 \end{aligned}$$

$$\begin{aligned} (W/L)_n &= 10 \\ (W/L)_p &= 20 \end{aligned}$$

The power supply voltage is 5 V , and the output load capacitance is 1.5 pF . Calculate the rise time and the fall time of the output signal using (i) exact method (differential equations) (ii) average current method