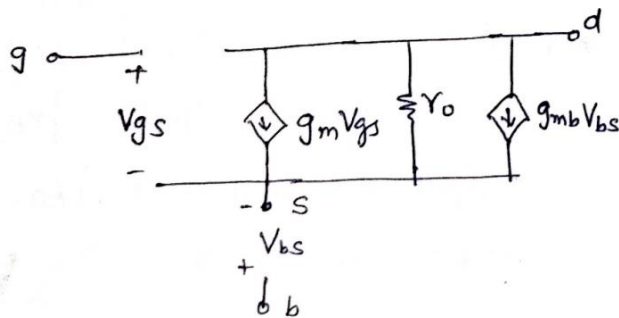


Solution: Tutorial Sheet-8

- 1) Draw the low frequency small signal model for n-Channel MOS transistor.
Derive the expressions for model parameters.

= Low frequency small signal model of nmos transistor



g_m = trans conductance parameter
~~parameter~~

r_o = Resistance due to c.m effect

g_{mb} = transconductance parameter
(it is due to body bias effect)

g_m in triode/linear region:-

$$I_{DS} = \frac{K_n}{2} [2(V_{GS} - V_{th,n})V_{DS} - V_{DS}^2]$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}}$$

$$= \frac{K_n}{2} [2(1-0)V_{DS} - 0]$$

$$\boxed{g_m = K_n V_{DS}} \quad (\text{for linear region})$$

g_m in satⁿ region:-

$$I_{os} = \frac{K_n}{2} (V_{GS} - V_{to,n})^2$$

$$g_m = \frac{\partial I_{os}}{\partial V_{GS}} = \frac{K_n}{2} \cdot 2(V_{GS} - V_{to,n})$$

$$\boxed{g_m = K_n (V_{GS} - V_{to,n})}$$

$$g_m = K_n V_{OV}$$

where

$$V_{OV} = V_{GS} - V_{to,n}$$

↳ It is overdrive voltage.

Parameter r_o :-

→ It is present in only satⁿ region because CLM effect occurs in satⁿ region.

$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}}$$

$$I_{os} = \frac{K_n}{2} (V_{GS} - V_{to}) (1 + \lambda V_{DS})$$

$$\frac{\partial I_{os}}{\partial V_{DS}} = \frac{K_n}{2} (V_{GS} - V_{to,n}) \lambda \approx \lambda I_{os}$$

$$\Rightarrow \boxed{r_o = \frac{1}{\lambda I_{os}}}, I_{os} \approx \frac{K_n}{2} (V_{GS} - V_{to,n})^2$$

g_{mb} : In satⁿ region.

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{tn})^2$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$= \frac{K_n}{2} \cdot 2(V_{GS} - V_{tn}) \cdot \left(-\frac{\partial V_{tn}}{\partial V_{BS}}\right)$$

$$= g_m \frac{\partial V_{tn}}{\partial V_{SB}} \left[\because V_{BS} = -V_{SB} \right]$$

We know that

$$V_{tn} = V_{t0,n} + \gamma \left[\sqrt{|-2\phi_f| + V_{SB}} - \sqrt{|-2\phi_f|} \right]$$

$$\frac{\partial V_{tn}}{\partial V_{SB}} = 0 + \gamma \left[\frac{1}{2} \frac{1}{\sqrt{|-2\phi_f| + V_{SB}}} - 0 \right]$$

$$= \frac{\gamma}{2\sqrt{|-2\phi_f| + V_{SB}}}$$


$$\Rightarrow \boxed{g_{mb} = \frac{g_m}{2} \cdot \frac{\gamma}{\sqrt{|-2\phi_f| + V_{SB}}}}$$

2) Determine the values of small signal parameters for the n-channel MOSFET with the following biasing conditions:

a. $V_D=5V$, $V_S=1V$, $V_B=1V$, $V_G=3V$.

b. $V_D=5V$, $V_S=2V$, $V_B=1V$, $V_G=3V$.

Use $|2\phi_f| = 0.6V$, $\gamma = 0.4 V^{1/2}$, $\lambda = 0.1$ per volt, $\mu_n C_{ox} = 25mA/V^2$, $W/L=15$ and $V_{t0} = 1V$.

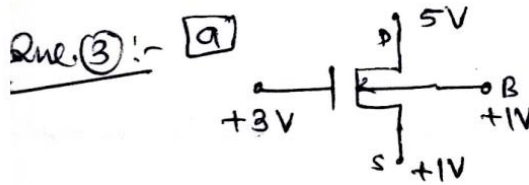

$$V_{GS} \geq V_{t0} \quad \text{for ON.}$$

$$3V \geq 1V, \quad \text{True}$$

$$\text{for sat}^n, \quad V_{DS} \geq V_{GS} - V_{t0,n}$$

$$5V \geq 3V - 1V$$

$$4 \geq 2, \quad \text{cond}^n \text{ is satisfied.}$$

Device is operating in satⁿ.

$$\begin{aligned} (i) \quad g_m &= k_n (V_{GS} - V_{t0,n}) \\ &= \mu_n C_{ox} \frac{W}{L} (3V - 1V) \\ &= 25 \times 10^{-3} \times 15 \times 1 \\ g_m &= 375 \text{ mA/V} \end{aligned}$$


$$\begin{aligned}
 (i) \quad I_{DQ, \text{sat}} &= \frac{K_n}{2} (V_{GS} - V_{to})^2 \\
 &= \frac{25 \times 10^{-3} \times 15}{2} (3 - 1)^2 \\
 &= 187.5 \text{ mA}
 \end{aligned}$$

$$r_o \approx \frac{1}{0.1 \times 187.5 \times 10^{-3}}$$

$$r_o \approx 533 \Omega$$

$$(ii) \quad g_{mb} = 0, \text{ since } V_{SB} = 0.$$

Q.3(b)!

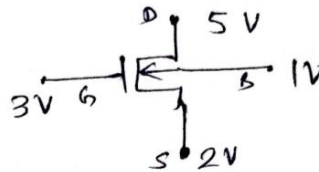

$$V_{SB} = 2 - 1 = 1 \text{ V}$$

$$\begin{aligned}
 V_{to} &= V_{to} + \gamma \left[\sqrt{1 - 2\phi_f + V_{SB}} - \sqrt{1 - 2\phi_f} \right] \\
 &= 1 + 0.4 \left[\sqrt{0.6 + 1} - \sqrt{0.6} \right] \\
 &= 1 + 0.4 \left[1.2649 - 0.774 \right] \\
 &= 1.19636 \text{ V}
 \end{aligned}$$

$$g \quad V_{GS} = 3 - 2 \geq 1.19 \quad \text{ON}$$

$$\text{Since, } V_{GS} > V_{to}$$

$$\Rightarrow \text{Transistor is ON}$$

$$V_{GS} < 1.19 \text{ (Transistor is OFF)}$$

$$g_m = 0$$

$$r_o = \infty$$

$$g_{mb} = 0$$

- 3) Find the small signal voltage gain, input and output resistances of the common source amplifier with resistive load.

Sol.: Using small signal low frequency model, you may derive the followings

$$\text{Voltage gain} = -g_m(r_o || R_D)$$

$$\text{Output Resistance} = r_o || R_D$$

$$\text{Input resistance} = \infty$$

- 4) In the circuit of Fig. 1, determine the small signal low-frequency voltage gain, input resistance and output resistance. Consider $V_{GG} = 4.4 \text{ V}$, $k_n = 0.25 \text{ mA/V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $V_{SB} = 0 \text{ V}$.


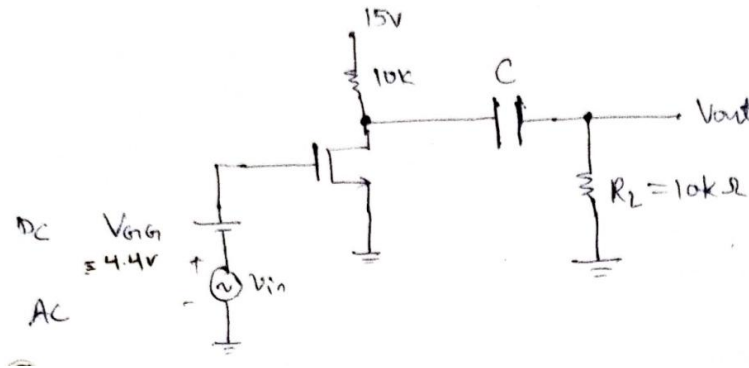


Fig. 1

DC equivalent CKT:-

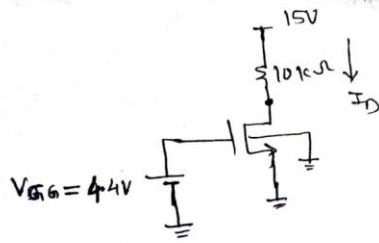

$$I_D = \frac{k_n}{2} (V_{GS} - V_t)^2$$

(neglected CLM effect
for simplicity)

$$I_D = \frac{0.25 \times 10^{-3}}{2} (4.4 - 1.5)^2$$

$$I_D = 1.051 \text{ mA}$$

$I_D =$

$$I_D = \frac{15 - V_D}{10k}$$

$$V_D = 15 - 10 \times 10^3 \times I_D$$

$$= 15 - 10 \times 1.051$$

$$V_D = 4.49 \text{ V}$$

Satn condn:

$$V_{DS} \geq V_{GS} - V_{t0}$$

$$4.49 \geq 4.4 - 1.5 \quad \checkmark$$

→ Calculated values are correct.

$$g_m = k_n (V_{GS} - V_{t0})$$

$$g_m = 0.25 (4.4 - 1.5) \text{ mA/V}$$

$$g_m = 0.725 \text{ mA/V}$$

$$\text{Overdrive } v_D \text{ } t_{avg} = V_{GS} - V_{t0}$$

$$r_o = \frac{1}{\lambda I_D}$$




$$= \frac{1}{0.02 \times 1.051 \times 10^{-3}}$$

$$r_o = 47.57 \text{ k}\Omega$$

AC analysis:

Deactivate all the dc sources.

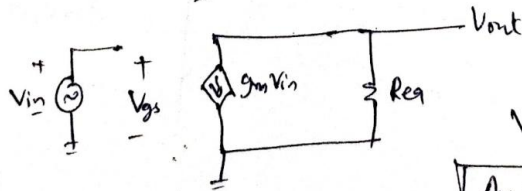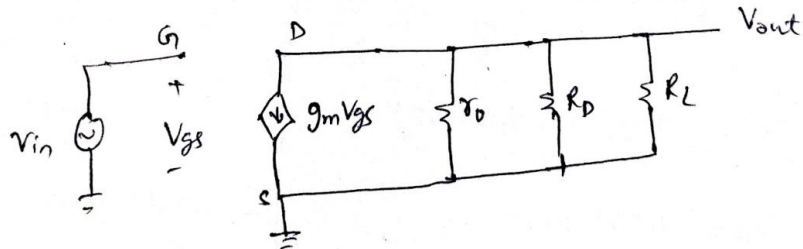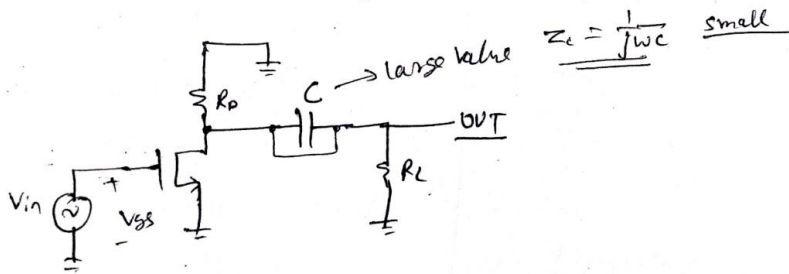- ~~Remove all the dc sources from the circuit.~~
- Assume coupling capacitors are sufficiently large so act as short circuits at the signal frequencies of interest.



$$V_{out} = -g_m V_{in} \times R_{eq}$$

$$A_v = -g_m R_{eq} \quad R_{eq} = R_D || R_L || r_o$$

$$R_{eq} = 10 \parallel 10 \parallel 47.57 = 5 \parallel 47.57 \\ = 4.13 \text{ k}\Omega$$


$$A_v = -g_m R_{eq} = 0.725 \times 4.13 = \underline{\underline{-2.995}}$$

Input resistance:-

$$R_{in} = \infty$$

Output resistance:-

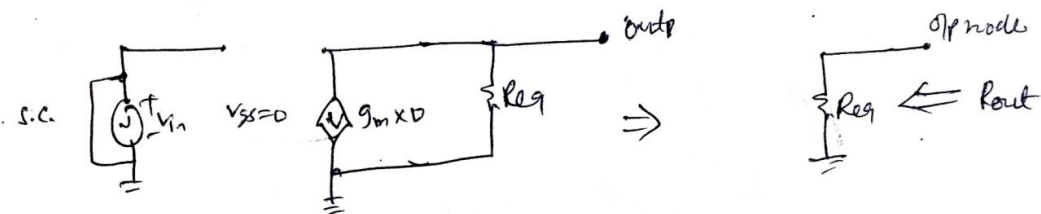- Deactive all the sources.
- Apply 1V source at the o/p and find current delivered by it.



$$R_{out} = (R_o \parallel R_D \parallel R_L) = 4.13 \text{ k}\Omega$$